

Front-end circuits

Choose yourself and new technologies

Project co-financed from the EU European Social Fund

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

References

- U. Tietze, Ch.Schenk, Electronics Circuits – Handbook for Design and Applications, Springer, 2008
- J.P. Bentley, Principles of measurement system, Pearson Education, 4th ed.
- Application notes of:
 - Linear Technology,
 - Analog Devices,
 - Texas Instruments,
 - National Semiconductors



Project co-financed from the EU European Social Fund

Wrocław University of Technology Master programmes in English at Wrocław University of Technology


outline

- operational amplifier
 - VV- voltage/voltage amp – review
 - CV – current/voltage
 - VC – voltage/current
 - CC – current/current
- electrometer
- charge amplifier
- chopped amp and parametric modulation amp
- auto-zero amp




Project co-financed from the EU European Social Fund

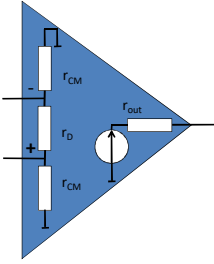
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




VV OPA




$$V_{OUT} = (V_P - V_N) k_{uD}$$




Project co-financed from the EU European Social Fund

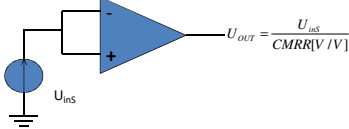
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




VV OPA - CMRR




$$U_{OUT} = \frac{U_{CM}}{CMRR[V/V]}$$

Project co-financed from the EU European Social Fund





Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

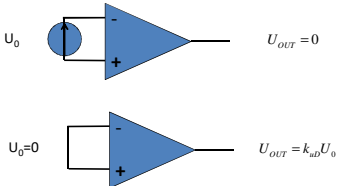
VV OPA – offset voltage




$$U_{OUT} = 0$$


$$U_{OUT} = k_{uD} U_0$$


Project co-financed from the EU European Social Fund





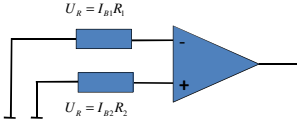
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology



VV OPA – polarization/offset current




$$U_{off} = \frac{U_{OUT}}{Rk_{uD}} = (I_{B1}R_1 - I_{B2}R_2) \approx I_{Boff}R_{av} + I_B\Delta R$$









Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Offset of a system Chalkboard










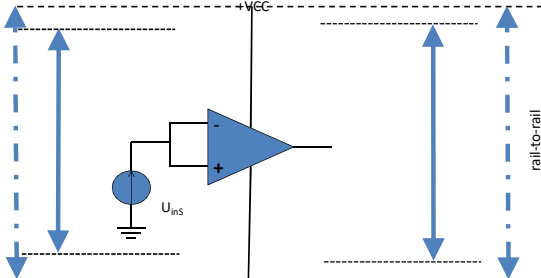

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




VV OPA – input/output voltage swing












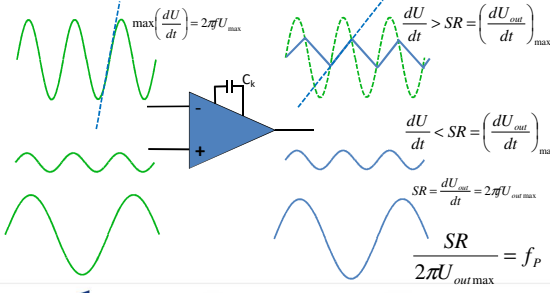
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




VV OPA – slew rate - SR




$\max\left(\frac{dU}{dt}\right) = 2\pi f U_{\max}$
 $\frac{dU}{dt} > SR = \left(\frac{dU_{out}}{dt}\right)_{\max}$
 $\frac{dU}{dt} < SR = \left(\frac{dU_{out}}{dt}\right)_{\max}$
 $SR = \frac{dU_{out}}{dt} = 2\pi f U_{out \max}$
 $\frac{SR}{2\pi U_{out \max}} = f_P$










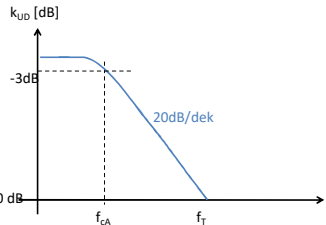
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




VV OPA bandwidth




$k_{UD} \text{ [dB]}$
 -3dB
 0 dB
 f_{CA}
 f_T
 20dB/dek










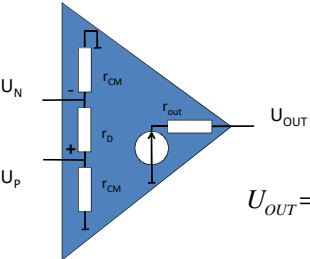
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




VV OPA




U_N
 r_{CM}
 r_D
 r_{CM}
 r_{out}
 U_P
 U_{OUT}
 $U_{OUT} = (U_P - U_N)k_{uD}$




Wrocław University of Technology



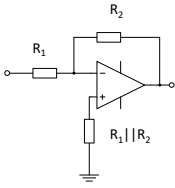
Master programmes in English
 at Wrocław University of Technology




inverting amplifier




$$K_u = \frac{U_{out}}{U_{in}} = -\frac{R_2}{R_1}$$




Wrocław University of Technology



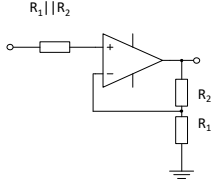
Master programmes in English
 at Wrocław University of Technology




Noninverted amplifier




$$K_u = \frac{U_{out}}{U_{in}} = 1 + \frac{R_2}{R_1}$$







Wrocław University of Technology

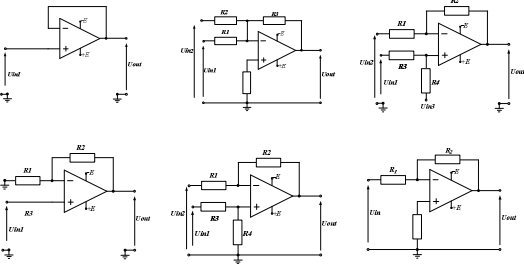Master programmes in English
 at Wrocław University of Technology



Numerical solutions






Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Calculations on the board








Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology



Application tips

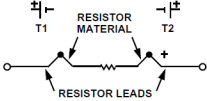


gain and offset drift




Error (voltage offset) is due to temperature difference of resistor (or any other component) terminals.


TYPICAL RESISTOR THERMOCOUPLE EMFs

- CARBON COMPOSITION 400µV/°C
- METAL FILM 20µV/°C
- EVENOHM OR MANGANIN 2µV/°C
- WIRE-WOUND 0.05µV/°C
- RCD COMPONENTS HP-SERIES



Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology






Application tips


RTI vs. RTO errors

Total Error, RTI = Input Error + (Output Error/Gain)
Total Error, RTO = (Gain * Input Error) + Output Error


VOLTAGE OFFSET	(Total RTI Error = $V_{OSI} + V_{OSO}/G$)		
Input Offset, V_{OSI}	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$	30	125
Over Temperature	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$		185
Average TC	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$	0.3	1.0
Output Offset, V_{OSO}	$V_S = \pm 15\text{ V}$	400	1000
	$V_S = \pm 5\text{ V}$		1500
Over Temperature	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$		2000
Average TC	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$	5.0	15
Offset Referred to the			

Total Offset Error RTI = $V_{OSI} + (V_{OSO}/G) = 30\mu\text{V} + (400\mu\text{V}/10) = 30\mu\text{V} + 40\mu\text{V} = 70\mu\text{V}$
Total Offset Error RTO = $(G(V_{OSI})) + V_{OSO} = (10(30\mu\text{V})) + 400\mu\text{V} = 700\mu\text{V}$










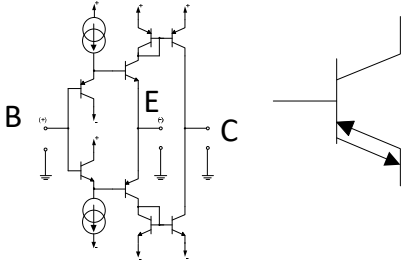
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




CC amplifier




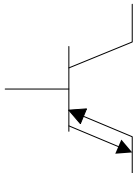
Project co-financed from the EU European Social Fund



Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology



CC – transistor like amplifier






Transistor like:


- $I_C = I_E$
- R_{in} = very high (base)
- R_{out} = very high (collector)

Differences:


- quiescent point is set internally
- I_C is positive (source)
- $U_{BEQ} = 0$ (and not 0.6V)
- I_C and I_B can be +/-


Project co-financed from the EU European Social Fund





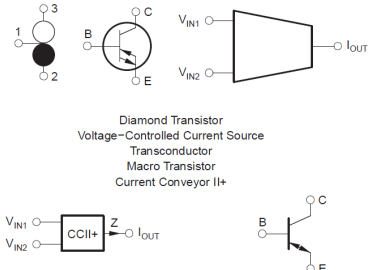
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




CC – alternative symbols and names




Diamond Transistor
Voltage-Controlled Current Source
Transconductor
Macro Transistor
Current Conveyor II+






Project co-financed from the EU European Social Fund


Wrocław University of Technology

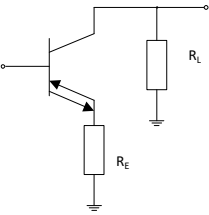


Master programmes in English
at Wrocław University of Technology







$$K_u = \frac{U_{out}}{U_{in}} = \frac{R_L}{R_E}$$

Tips:
K_u positive (in transistor negative)
Both R are small (10-1000Ω)

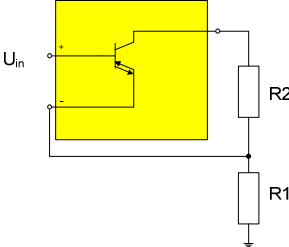

Wrocław University of Technology

Master programmes in English
at Wrocław University of Technology







CC amp – application

current feedback and current output




$$U_{out} = U_{in} \left(1 + \frac{R_2}{2R_1} \right)$$







Wrocław University of Technology



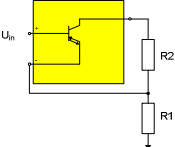
Master programmes in English
at Wrocław University of Technology




CC amp - application




CC	Current amp
Example	OPA615
Applications	h.f. filters, laser drivers, line drivers, magnetic heads (hard discs)
Advantages	High bandwidth High slew rate
Disadvantages	Load dependent parameters
Offset	8 mV !!!!!
Offset drift	40uV/deg
Bias current (+)	0,3uA
Large signal bandwidth	500MHz
Slew rate	3000V/us










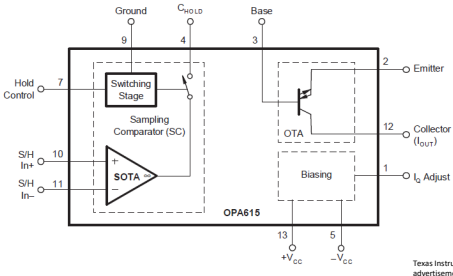
Master programmes in English
at Wroclaw University of Technology




CC amp –example- OPA615








Project co-financed from the EU European Social Fund


Texas Instruments advertisement materials





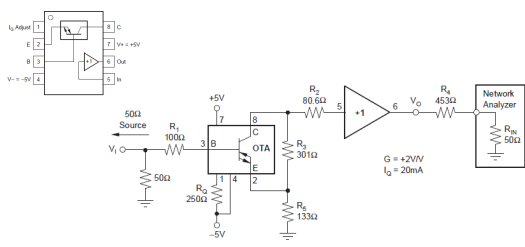
Master programmes in English
at Wroclaw University of Technology




CC amp –example- OPA860








Project co-financed from the EU European Social Fund


Texas Instruments advertisement materials





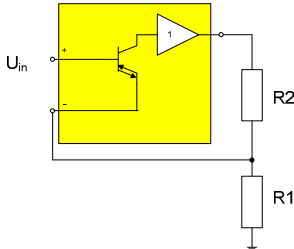
Master programmes in English
at Wroclaw University of Technology





CV – transimpedance amp current feedback, voltage output amp




$$U_{out} = U_{in} \left(1 + \frac{R_2}{R_1} \right)$$




Project co-financed from the EU European Social Fund




Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

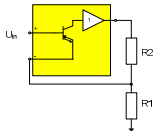
CV amp




CV	Transimpedance amp
Example	AD8024
Applications	line drivers, LCD drivers, Sallen-Key active filter
Advantages	High bandwidth High slew rate
Disadvantages	Can be unstable with C or L load
Offset	2 mV !!!!
Offset drift	2uV/deg
Bias current (+)	1uA
Large signal bandwidth	350MHz
Slew rate	2400V/us









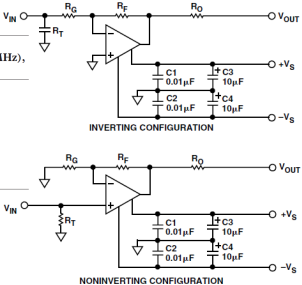

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology


AD8011 current feedback amp


Gain	R_F (Ω)	R_O (Ω)	R_T (Ω)	Small Signal -3 dB BW (MHz), $V_S = \pm 5$ V
-1	1000	1000	52.3	150
-2	1000	499	54.9	130
-10	499	49.9		140
+1	1000	1000	49.9	400
+2	1000	1000	49.9	250
+10	422	47.5	49.9	100
+6	1000	200	49.9	70
+6	500	100	49.9	170









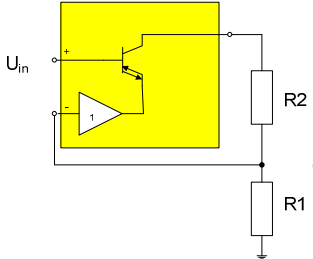


Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology


VC – transconductance amp voltage feedback current output




$$U_{out} = U_{in} \left(1 + \frac{R_2}{R_1} \right)$$










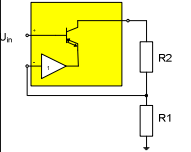
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




VC – transconductance amp




VC	Transconductance amplifier
Example	MAX4445
Applications	Capacitive load
Advantages	Low offset and drift Stable with C load
Disadvantages	Load dependent gain
Offset	15 mV !!!!
Offset drift	12uV/deg
Bias current (+)	10uA
Large signal bandwidth	550MHz
Slew rate	5000V/us


Project co-financed from the EU European Social Fund





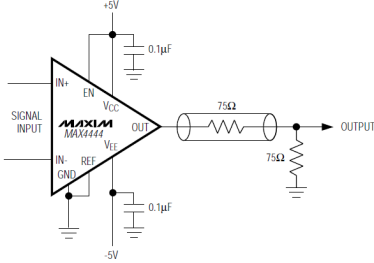
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




VC – transconductance amp




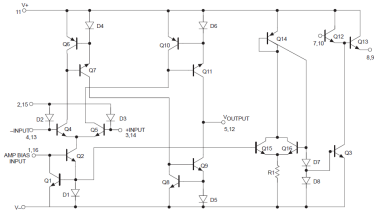
Project co-financed from the EU European Social Fund






Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology





On the board explanation








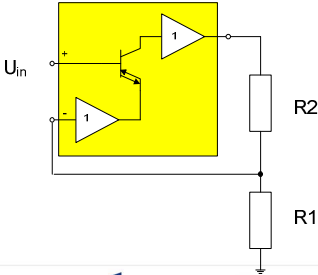Project co-financed from the EU European Social Fund





Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology





VV –traditional OPA



$$U_{out} = U_{in} \left(1 + \frac{R_2}{R_1} \right)$$

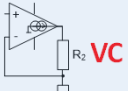

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology



Current output

➡


Voltage feedback





VC


Voltage output

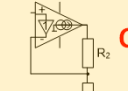
➡

Current feedback

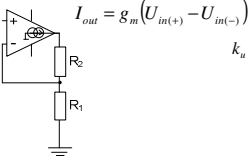

VV


Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology







TRANSCONDUCTANCE AMP (VC)




$$I_{out} = g_m (U_{in(+)} - U_{in(-)})$$

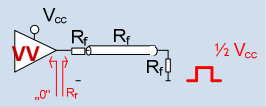
$$k_u = \frac{U_{out}}{U_{in}} = \left(\frac{g_m R_L R_1}{1 + g_m R_L \frac{R_1}{(R_1 + R_2)}} \right) \approx \left(1 + \frac{R_2}{R_1} \right)$$










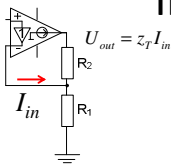Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology







TRANSIMPEDANCE AMP (CV)



$$U_{out} = z_T I_{in}$$
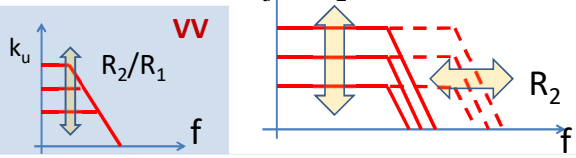
$$k_u = \frac{U_{out}}{U_{in}} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{1}{1 + \frac{R_2}{z_T}}\right) \approx \left(1 + \frac{R_2}{R_1}\right)$$

$$z_T = \frac{R_T}{1 + j \frac{f}{f_g}} \Rightarrow f_{gf} = 1 + \frac{R_T}{R_2}$$





Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Transimpedance amp as photodiode front-end







Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology







Electrometer

electronic device for charge or potential (voltage) measurements with very little leakage current, down to fA;


Used for example in measurements of:

- pH,
- redox potential (oxidation, reduction potential , ORP),
- ionization radiation (ionization chamber),
- piezosensors (e.g. acceleration),
-



Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology







Types of electrometers:

Valve electrometer – use a special tube of leakage of fA;


Solid state – with FET/MOSFET transistors;

Vibrating capacitor – („parametric modulation“)



Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology







Electrometer problems:

Use of GΩ resistors (Vishay)


Surface leakage (PCB on teflon, glass, cleaning problems, drying),

Transistor/IC leakage,








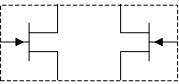Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology










High input impedance



LS830 2 FET in common case:
 $I_g < 80\text{fA}$, $E_n < 70\text{nV}/\text{Hz}^{1/2}$, $C < 3\text{pF}$

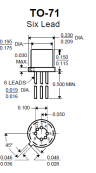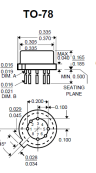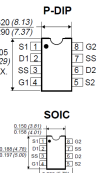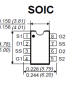Single FET:
BF862 (3pA)
2N4416 ($C < 1\text{pF}$)

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

Surface leakage solutions

INVERTING AMPLIFIER

NONINVERTING AMPLIFIER

EXTERNAL CAPACITORS
OUTPUT GUARD
EXTERNAL CAPACITORS
INPUT GUARD

HUMAN CAPITAL
Investing in the future

Wrocław University of Technology

Project co-financed from the EU European Social Fund

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

LTC6078/LTC6079 by Linear Technology

Maximum Offset Voltage of 25 μ V (25 $^{\circ}$ C)

- Maximum Offset Drift of 0.7 μ V/ $^{\circ}$ C
- Maximum Input Bias: 1pA (25 $^{\circ}$ C) 50pA (\leq 85 $^{\circ}$ C)
- Micropower: 54 μ A per Amp
- 95dB CMRR (Min)
- 100dB PSRR (Min)
- Input Noise Voltage Density: 16nV/ \sqrt Hz
- Rail-to-Rail Inputs and Outputs
- 2.7V to 5.5V Operation Voltage
- LTC6078 Available in 8-Lead MSOP and 10-Lead DFN
- Packages; LTC6079 Available in 16-Lead SSOP and DFN Packages

HUMAN CAPITAL
Investing in the future

Wrocław University of Technology

Project co-financed from the EU European Social Fund

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology


Driven Shield Inputs - example

HUMAN CAPITAL
Investing in the future


Wrocław University of Technology

Project co-financed from the EU European Social Fund


15





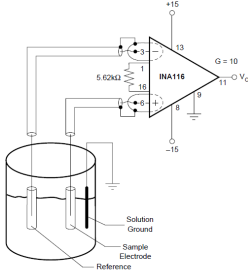
Master programmes in English
at Wrocław University of Technology




pH transducer




Project co-financed from the EU European Social Fund







Master programmes in English
at Wrocław University of Technology




LTC6078/LTC6079 application example

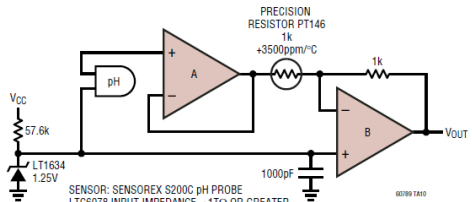pH Probe Amplifier




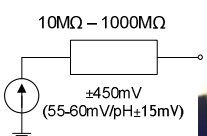
Project co-financed from the EU European Social Fund





Master programmes in English
at Wrocław University of Technology






pH glass electrode construction

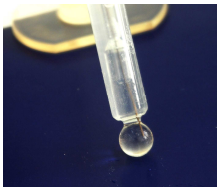

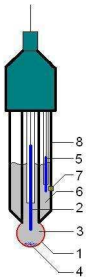








Project co-financed from the EU European Social Fund

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

pH glass electrode construction

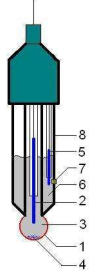
- 1.a sensing part of electrode, a bulb made from a specific glass
- 2.internal electrode, usually silver chloride electrode or calomel electrode
- 3.internal solution, usually a pH=7 buffered solution of 0.1 mol/L KCl for pH electrodes or 0.1 mol/L MeCl for pMe electrodes
- 4.when using the silver chloride electrode, a small amount of AgCl can precipitate inside the glass electrode
- 5.reference electrode, usually the same type as 2
- 6.reference internal solution, usually 0.1 mol/L KCl
- 7.junction with studied solution, usually made from ceramics or capillary with asbestos or quartz fiber.
- 8.body of electrode, made from non-conductive glass or plastics.



HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

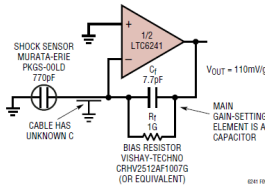LTC6241 „charge amplifier” (integrating amplifier)




SHOCK SENSOR MURATA-ERIE PK85-R0LD 770pF
CABLE HAS UNKNOWN C
BIAS RESISTOR VISHAY-TECHNO CRHV2512AF1007G (OR EQUIVALENT)
MAIN GAIN-SETTING ELEMENT IS A CAPACITOR
V_{out} = 110mV/g

Linear Technology advertisement materials

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

An idea of „charge amplifier”

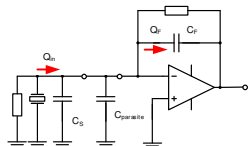


$$Q_{in} = Q_F$$

$$\text{as } V_+ = V_-$$


$$U_{out} = U_{CF} = \frac{Q_F}{C_F}$$

U_{out} is not depend on C_s nor C_{parasite}


HUMAN CAPITAL Wrocław University of Technology





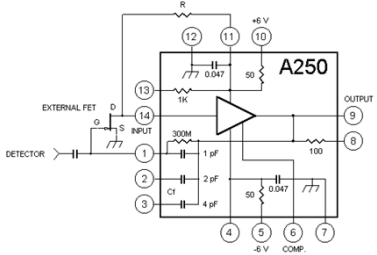
Wroclaw University of Technology
Master programmes in English
at Wroclaw University of Technology




A250 Amptek charge amp




AMPTEC advertisement materials










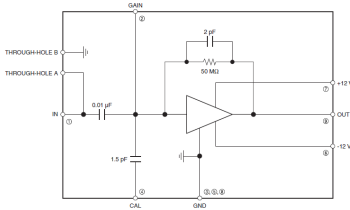
Wroclaw University of Technology
Master programmes in English
at Wroclaw University of Technology




Hybrid charge amplifier




Hamamatsu advertisement materials










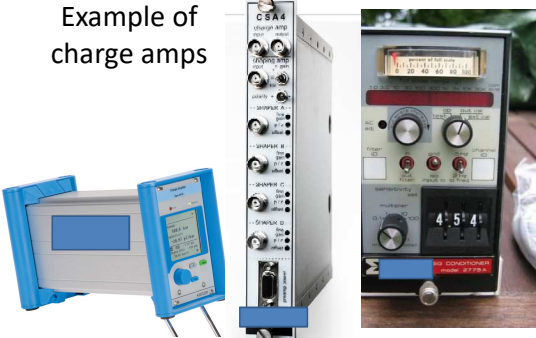
Wroclaw University of Technology
Master programmes in English
at Wroclaw University of Technology




Example of charge amps




Hamamatsu advertisement materials










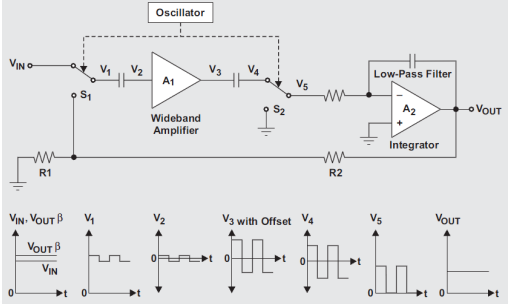
Master programmes in English
at Wrocław University of Technology




An idea of chopper amp




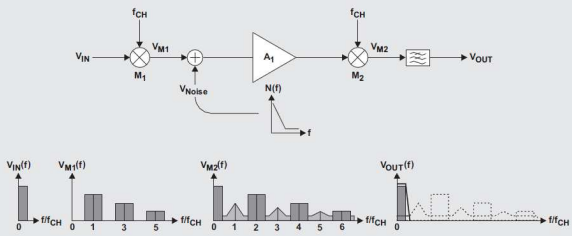
Project co-financed from the EU European Social Fund






Master programmes in English
at Wrocław University of Technology




An idea of chopper amp in frequency domain




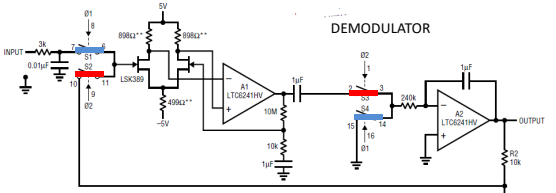
Project co-financed from the EU European Social Fund



Master programmes in English
at Wrocław University of Technology






DEMODULATOR



* = 0.1% METAL FILM RESISTOR
** = 1% METAL FILM RESISTOR
C = LTC201 QUAD
= LSC389
= LINEAR INTEGRATED SYSTEMS
FREMONT, CA

NOISE = 40nV/√Hz TO 10Hz
OFFSET = 1μV
DRIFT = 0.5μV/°C
GAIN = 10
OPEN-LOOP GAIN = 10⁵
I_{BAS} = 500pA

Linear Technology advertisement materials

Project co-financed from the EU European Social Fund

[illegible]

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

chopper -stabilized amp

chopper amp

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

auto-zero amp

phase 1

$$V_{C1} = V_{OSN} \left(\frac{A_N}{1 + B_N} \right)$$

phase 2

$$V_{C2} = A_N (V_{IN} + V_{OSN}) - B_N V_{C1}$$

$$V_{C2} = A_N \left(V_{IN} + \frac{V_{OSN}}{1 + B_N} \right)$$

$$V_{OUT} = A_M (V_{IN} + V_{OSN}) + B_M V_{C2}$$

$$V_{OUT} = V_{IN} (A_M + A_N B_M) + V_{OSN} A_M + V_{OSN} \left(\frac{A_N B_M}{1 + B_N} \right) = V_{IN} A_N B_M \left(1 + \frac{A_M}{A_N B_M} + V_{OSN} \frac{A_M}{A_N B_M} + V_{OSN} \frac{1}{1 + B_N} \right)$$

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

$$V_{OUT} = V_{IN} (A_M + A_N B_M) + V_{OSM} A_M + V_{OSN} \left(\frac{A_N B_M}{1 + B_N} \right) =$$

$$= V_{IN} A_N B_M \left(1 + \frac{A_M}{A_N B_M} + V_{OSM} \frac{A_M}{A_N B_M} + V_{OSN} \frac{1}{1 + B_N} \right) \approx$$

$$= V_{IN} AB + A(V_{OSM} + V_{OSN}) = AB \left(V_{IN} + \frac{V_{OSM} + V_{OSN}}{B} \right)$$

HUMAN CAPITAL Wrocław University of Technology

Intersil (Maxim)
advertisement materials





*NOTE: Internal capacitors. No external capacitors required.






10






Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology


Summary

- operational amplifier
 - ✓VV- voltage/voltage amp – review
 - ✓CV
 - ✓VC
 - ✓CC
- electrometer
- charge amplifier
- choppered and auto-zero amp
- parametric modulation









Project co-financed from the EU European Social Fund


Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

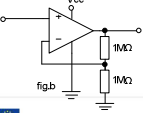
Test questions:

1. The amplifier was designed for video signal using “current feedback amplifier”. What is wrong with it ? (fig.b) ?
2. What are the VV, CC, CV, VC op-amp ?
3. What are the main features of a transconductance and a transimpedance amplifier?
4. What is the idea of a charge amplifier ?
5. What is the idea of a chopper amplifier ?
6. What is the idea of a parametric modulation amp ?



Project co-financed from the EU European Social Fund
