

Measurement circuits and systems

instrumentation and differential amplifiers

Choose yourself and new technologies





Project co-financed from the EU European Social Fund



Wrocław University of Technology


Master programmes in English
at Wrocław University of Technology




References

C. Kitchin, L. Counts,
A Designer's Guide To Instrumentation Amplifiers,
Analog Devices,3rd edition, 2006

<https://www.analog.com/en/education/education-library/dh-designers-guide-to-instrumentation-amps.html>






Project co-financed from the EU European Social Fund






Wrocław University of Technology

Master programmes in English
at Wrocław University of Technology




outline:


1. Introduction: understanding IN-AMP
2. IN-AMP inside
3. monolithic in-amps review
 - auto-zeroing amps
4. monolithic dif-amps review
5. application tips
6. application circuits
7. summary

Project co-financed from the EU European Social Fund






Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




instrumentation amplifier (in-amp)


- Not all amplifiers used in instrumentation applications are instrumentation amplifiers,
- and by no means are all in-amps used only in instrumentation applications.

In-amps are used in many applications, from motor control to data acquisition to automotive. The intent of this guide is to explain the fundamentals of what an instrumentation amplifier is, how it operates, and how and where to use it. In addition, several different categories of instrumentation amplifiers are addressed in this guide.







Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




in-amps vs. op-amps: what are the differences?

IN-AMP	OP-AMP
Internal closed-loop gain	closed-loop gain is determined by external resistors
Gain adjust resistor(s) is not connected with any input	Loop resistors affect input impedance (can change the input resistance)




Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Op-amps features

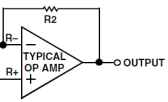$R_{IN} = R_1 (= 1k\Omega \text{ TO } 1M\Omega)$
 $GAIN = R_2/R_1$






$R_{IN} = R_+ (= 10^5\Omega \text{ TO } 10^{12}\Omega)$
 $GAIN = 1 + (R_2/R_1)$

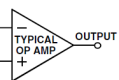A MODEL SHOWING THE INPUT RESISTANCE OF A TYPICAL OP AMP OPERATING AS AN INVERTING AMPLIFIER—AS SEEN BY THE INPUT SOURCE



A MODEL SHOWING THE INPUT RESISTANCE OF A TYPICAL OP AMP IN THE OPEN-LOOP CONDITION
 $(R_-) = (R_+) = 10^5\Omega \text{ TO } 10^{12}\Omega$

OP AMP INPUT CHARACTERISTICS






2




In-amp properties

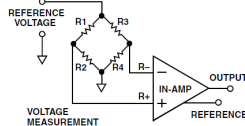THE VERY HIGH VALUE, CLOSELY MATCHED INPUT RESISTANCES CHARACTERISTIC OF IN-AMPS MAKE THEM IDEAL FOR MEASURING LOW LEVEL VOLTAGES AND CURRENTS—WITHOUT LOADING DOWN THE SIGNAL SOURCE.



IN-LINE CURRENT MEASUREMENT

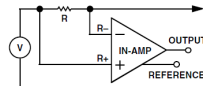

THE INPUT RESISTANCE OF A TYPICAL IN-AMP IS VERY HIGH AND IS EQUAL ON BOTH INPUTS. INPUT CURRENT IS LOW, SUCH THAT $I_B \times R$ CREATES A NEGLIGIBLE ERROR VOLTAGE.
 $R^- = R^+ = 10^9 \Omega$ TO $10^{12} \Omega$



IN-AMP INPUT CHARACTERISTICS



Project co-financed from the EU European Social Fund




CMRR in-amp vs. op_amp

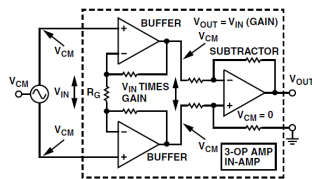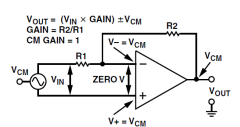


Project co-financed from the EU European Social Fund



Differential Amplifiers (not an in-amp)

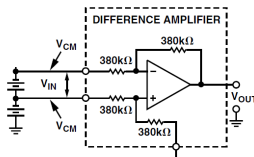

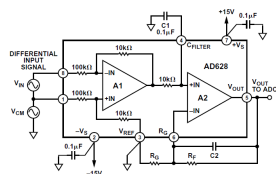- limited input resistance
- V_{CM} can be higher than supply voltage of the amp



Project co-financed from the EU European Social Fund




In-amp applications

- Data Acquisition
- Medical Instrumentation (EEG, EEC)
- Monitor and Control Electronics (current, voltage monitoring)
- Power Control Applications
- Audio Applications (very high CMRR vs. frequency)
- High Speed Signal Conditioning (including video signals) ??





common mode and differential signals

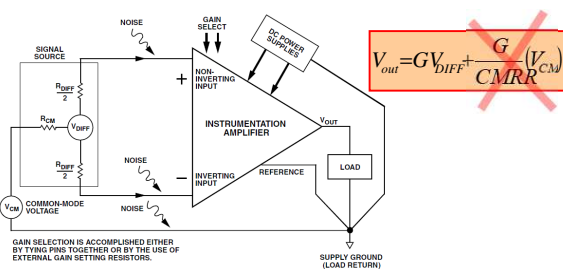





in-amp properties

- High AC (and DC) Common-Mode Rejection
- Low Offset Voltage and Offset Voltage Drift (1 μ V/deg to 10 μ V/deg)
- A Matched, High Input Impedance
- Low Input Bias and Offset Current Errors (pA)
- Low Noise -10 nV/ $\sqrt{\text{Hz}}$ @ 1 kHz (gain > 100)
- Low Nonlinearity (0.01% or better)
- Simple Gain Selection
- Adequate Bandwidth (up to 5MHz)
- Differential to Single-Ended Conversion
- Rail-to-Rail Input and Output Swing (often)
- Power vs. Bandwidth, Slew Rate, and Noise (disadvantage – power desipation)






Master programmes in English
at Wrocław University of Technology



INSIDE AN INSTRUMENTATION AMPLIFIER

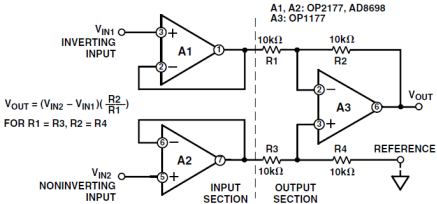





V_{IN1} INVERTING INPUT
 V_{IN2} NONINVERTING INPUT
 $V_{OUT} = (V_{IN2} - V_{IN1}) \left(\frac{R_2}{R_1} \right)$
 FOR $R_1 = R_3, R_2 = R_4$

A1, A2: OP2177, AD8698
 A3: OP1177


INPUT SECTION OUTPUT SECTION

A subtractor circuit with input buffering.








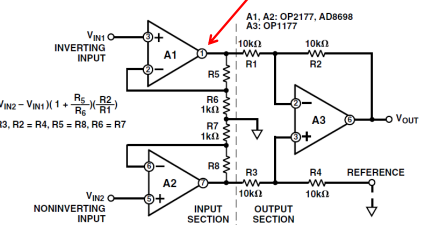Master programmes in English
at Wrocław University of Technology



in-amp inside cont.






V_{IN1} INVERTING INPUT
 V_{IN2} NONINVERTING INPUT
 $V_{OUT} = (V_{IN2} - V_{IN1}) \left(1 + \frac{R_5}{R_6} \cdot \frac{R_2}{R_1} \right)$
 FOR $R_1 = R_3, R_2 = R_4, R_5 = R_8, R_6 = R_7$


A1, A2: OP2177, AD8698
 A3: OP1177

INPUT SECTION OUTPUT SECTION


1 buffered subtractor circuit with buffer amplifiers operating with gain.


$$V_{o1} = \frac{V_{in1} + V_{in2}}{2} \cdot \frac{R_5}{R_6} = V_{CM} \cdot \frac{R_5}{R_6}$$



Master programmes in English
at Wrocław University of Technology



in-amp inside cont.

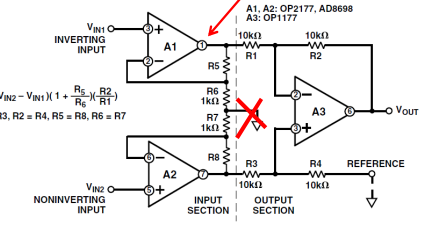




V_{IN1} INVERTING INPUT
 V_{IN2} NONINVERTING INPUT
 $V_{OUT} = (V_{IN2} - V_{IN1}) \left(1 + \frac{R_5}{R_6} \cdot \frac{R_2}{R_1} \right)$
 FOR $R_1 = R_3, R_2 = R_4, R_5 = R_8, R_6 = R_7$


A1, A2: OP2177, AD8698
 A3: OP1177

INPUT SECTION OUTPUT SECTION


1 buffered subtractor circuit with buffer amplifiers operating with gain.

$$V_{o1} = \frac{V_{in1} + V_{in2}}{2} \cdot \frac{R_5}{R_6} = V_{CM} \cdot \frac{R_5}{R_6}$$




Master programmes in English
at Wrocław University of Technology






in-amp inside cont.

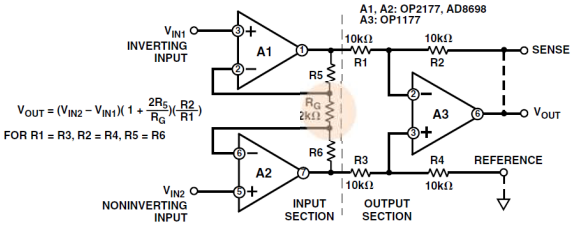
change of one resistor change the gain




$V_{OUT} = (V_{IN2} - V_{IN1}) \left(1 + \frac{2R_5}{R_6} \right) \left(\frac{R_2}{R_1} \right)$
 FOR $R_1 = R_3, R_2 = R_4, R_5 = R_6$

The classic 3-op amp in-amp circuit.








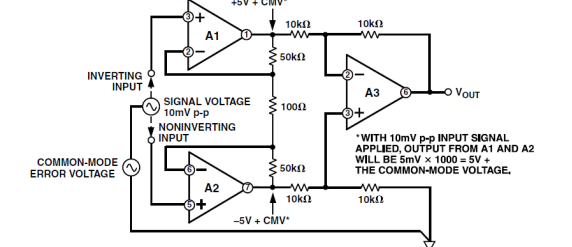Master programmes in English
at Wrocław University of Technology







Common Mode Voltage




WITH 10mV p-p INPUT SIGNAL APPLIED, OUTPUT FROM A1 AND A2 WILL BE 5mV × 1000 = 5V + THE COMMON-MODE VOLTAGE.

A 3-op amp in-amp showing reduced CMV range.








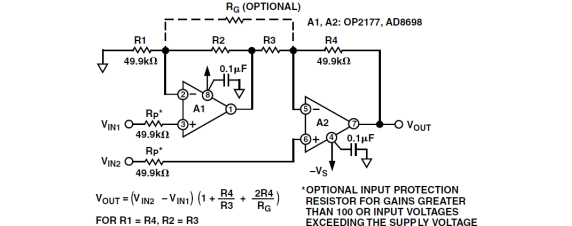Master programmes in English
at Wrocław University of Technology






simpler in-amp



$V_{OUT} = (V_{IN2} - V_{IN1}) \left(1 + \frac{R_4}{R_3} + \frac{2R_4}{R_Q} \right)$
 FOR $R_1 = R_4, R_2 = R_3$

*OPTIONAL INPUT PROTECTION RESISTOR FOR GAINS GREATER THAN 100 OR INPUT VOLTAGES EXCEEDING THE SUPPLY VOLTAGE

Figure 2-6. A 2-op amp in-amp circuit.

Master programmes in English
at Wrocław University of Technology

single supply consideration

Figure 2-8. Output swing limitations of 2-op amp in-amp using a 2.5 V reference.

$$V_{o1} = V_{CM} + (V_{CM} - V_{REF}) \frac{R_2}{R_1} \geq 0$$

????????

Master programmes in English
at Wrocław University of Technology

3op-amp vs. 2 op-amp

3op-amp	2 op-amp
Single supply can be easy applied.	Limited input voltages for single supply (1st stage can be working with negative output)
Signals from both inputs have the same path to output.	Lower CMRR (it comes from the inherent imbalance in the common-mode signal paths of the both inputs especially for high frequencies)

Master programmes in English
at Wrocław University of Technology

MONOLITHIC IN-AMPS

Table 3-1. Latest Generation Analog Devices In-Amps Summarized¹

Product	Features	Power Supply Current Typ	-3 dB BW Typ (G = 10)	CMR G = 10 (dB) Min Max	Input Offset Voltage Max	V _{OS} Drift (μV/°C) Max	RTI Noise ² (nV/√Hz) (G = 10)	Input Bias Current (nA) Max
AD8221	Precision, high BW	0.9 mA	560 kHz	100 ³	60 μV	0.4	11 max	1.5
AD620	General-purpose	0.9 mA	800 kHz	95 ³	125 μV	1	16 max	2
AD8225	Precision gain = 5	1.1 mA	900 kHz ⁴	83 ^{3,5}	150 μV	0.3	45 typ ⁶	1.2
AD8220	R-R, JFET input	750 μA	1500 kHz	100	250 μV	5	17 typ	10 pA
AD8222	Dual, precision, high BW	1.8 mA	750 kHz	100 ³	120 μV	0.4	11 max	2
AD8230	R-R, zero drift	2.7 mA	2 kHz	110	10 μV	10	240 typ	1
AD8250	High BW, programmable gain	3.5 mA	3.5 MHz	100	100 μV	1	13 typ	15
AD8251	High BW, programmable gain	3.5 mA	3.5 MHz	100	100 μV	1	13 typ	15
AD8553	Auto-zero with shutdown	1.1 mA	1 kHz	100	20 μV	0.1	150 typ	1
AD8555	Zero drift dig prog	2.0 mA	700 kHz ⁶	80 ⁶	10 μV	0.07	32 typ	22
AD8556	Dig prog IA with filters	2.0 mA	700 kHz ⁶	80 ⁶	10 μV	0.07	32 typ	54
AD622	Low cost	0.9 mA	800 kHz	86 ³	125 μV	1	14 typ	5
AD621	Precise gain	0.9 mA	800 kHz	93 ³	250 μV ⁷	2.5 ⁷	17 max ⁷	2
AD623	Low cost, S.S.	375 μA	800 kHz	90 ³	200 μV	2	35 typ	25
AD627	Micropower, S.S.	60 μA	80 kHz	100	250 μV	3	42 typ	10

NOTES

S.S. = single supply.

¹Refer to ADI website at www.analog.com for latest products and specifications.

²At 1 kHz. RTI noise = $\sqrt{(e_n)^2 + (i_n R_s)^2}$.


³For dc to 60 Hz, 1 kΩ source impedance.

⁴Operating at a gain of 5.


⁵For 10 kHz, 1 kΩ source impedance.

⁶Operating at a gain of 70.


⁷Referred to input (RTI).





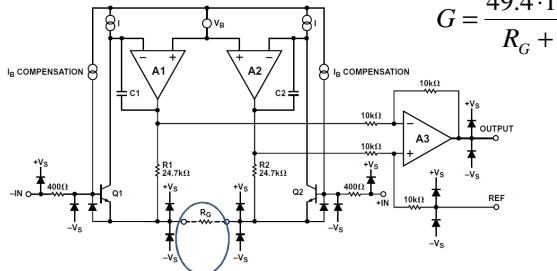
Master programmes in English
at Wrocław University of Technology





In-amp example




$$G = \frac{49.4 \cdot 10^3}{R_G + 1}$$




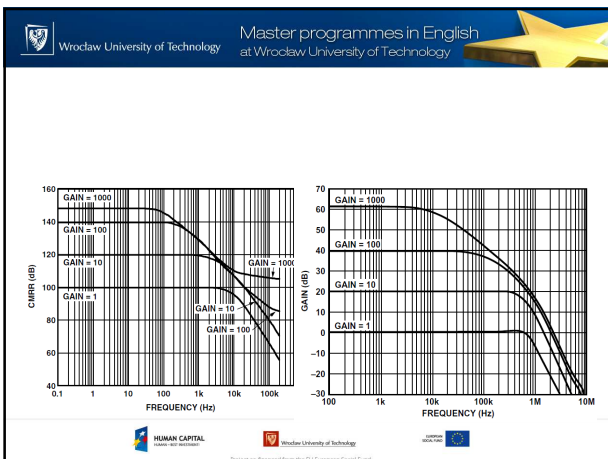

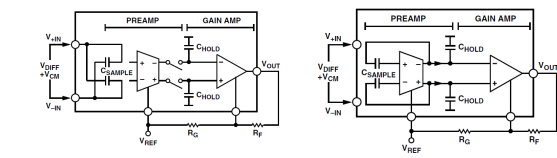Master programmes in English
at Wrocław University of Technology






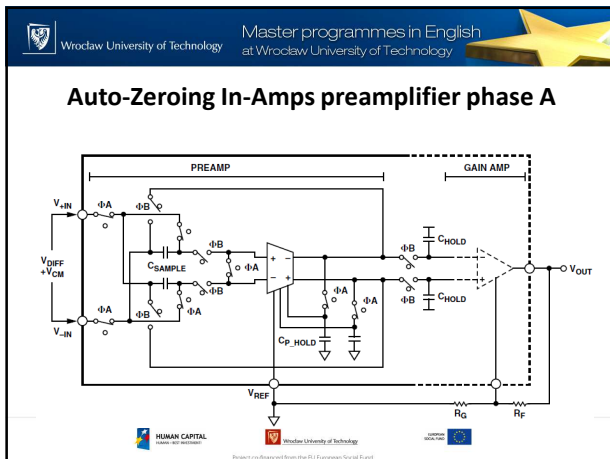
Auto-Zeroing Instrumentation Amplifiers (AD8230)





The differential component of the input signal is stored on sampling capacitors, C_{SAMPLE} . The gain amp conditions the signal stored on the hold capacitors, C_{HOLD} . Gain is set with the R_G and R_F resistors.

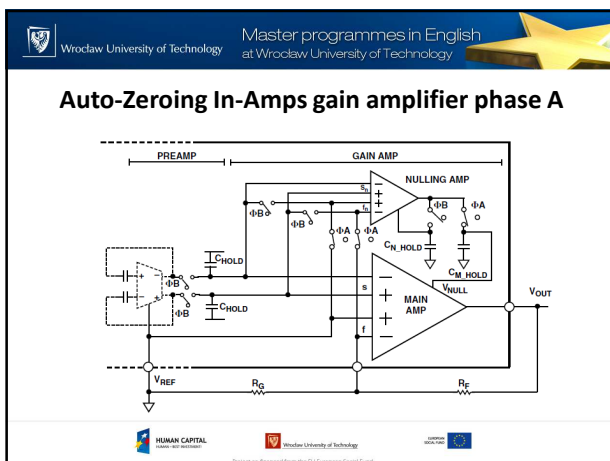
The differential signal is transferred to the hold capacitors, refreshing the value stored on C_{HOLD} . The gain amp continues to condition the signal stored on the hold capacitors, C_{HOLD} .









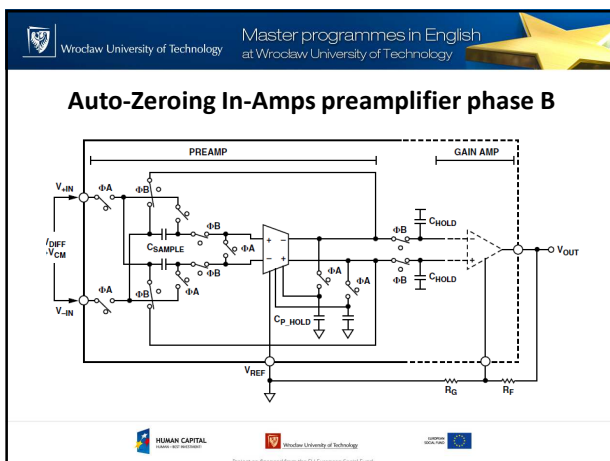


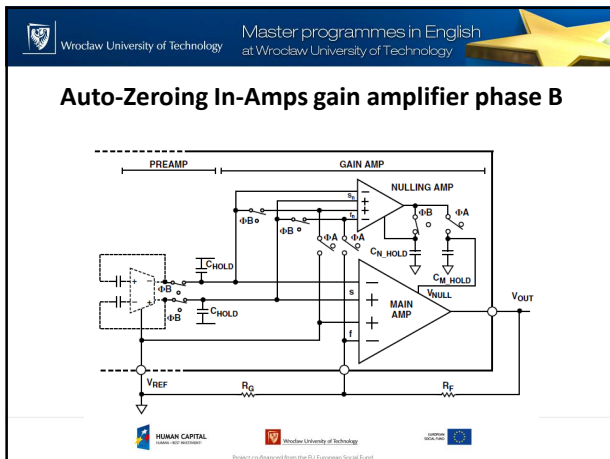


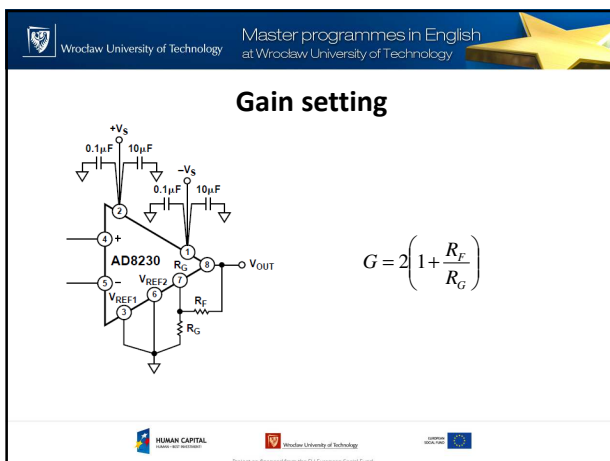




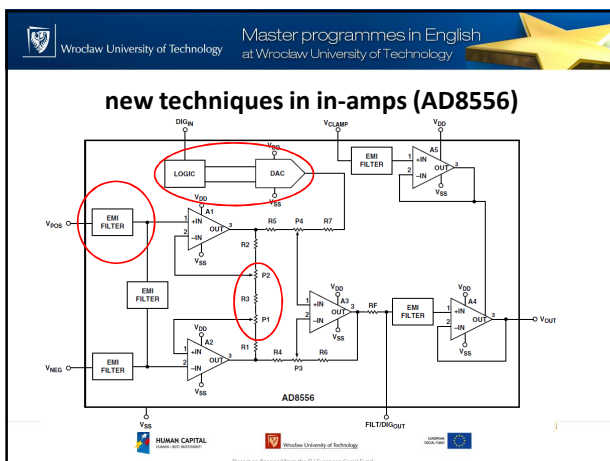

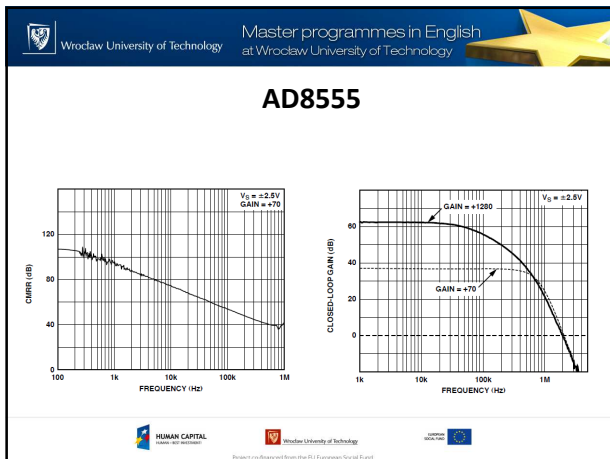

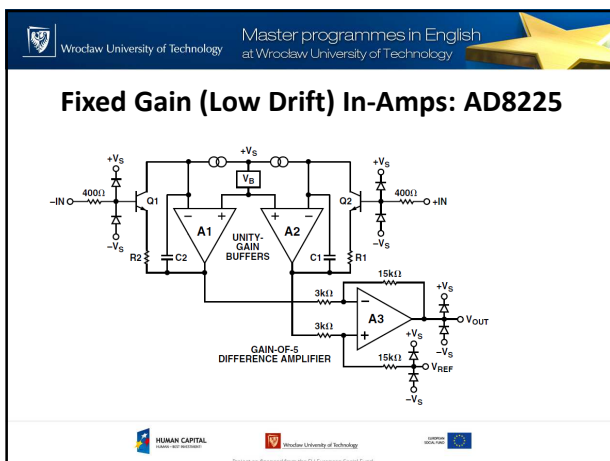

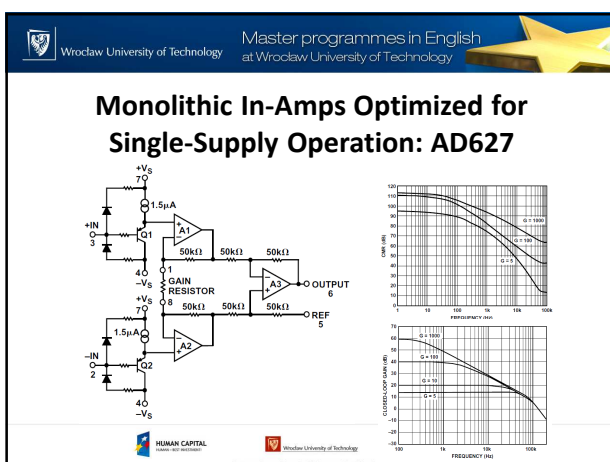


MONOLITHIC DIFFERENCE AMPLIFIERS

Table 4-1. Latest Generation of Analog Devices Difference Amps Summarized¹


Product	Features	Power Supply Current Typ	-3 dB BW Typ (G = 10)	CMR G = 10 (dB) Min	Input Offset Voltage Max	V _{os} Drift (μV/°C) Max	RTI Noise ² (nV/√Hz) (G = 10)
AD8202	S.S., 28 V CMV, G = 20	250 μA	50 kHz	80 ^{3,4,5}	1 mV ⁶	10	300 typ ³
AD8203	S.S., 28 V CMV, G = 14	250 μA	60 kHz ²	80 ^{5,7}	1 mV ⁶	10	300 typ ⁷
AD8205	S.S., 65 V CMV, G = 50	1 mA	50 kHz ²	80 ^{4,5,6}	2 mV ⁶	15 typ	500 typ ⁸
AD8206	S.S., 65 V CMV, G = 20	1 mA	100 kHz ²	76 ^{5,9}	2 mV ⁶	15 typ	500 typ ⁹
AD8210	S.S., current shunt monitor	500 μA	500 kHz ⁵	100 ^{3,5}	1 mV ⁶	5 typ	80 typ ¹
AD8212	Adjustable gain; CMV up to 500 V ¹⁰	200 μA	500 kHz	90	1 mV	10	100 typ
AD8213	Dual channel	1.3 mA ¹¹	500 kHz	100	1 mV	10	70 typ
AD8130	270 MHz receiver	12 mA	270 MHz	83 ^{12,13}	1.8 mV	3.5 mV	12.5 typ ^{12,14}
AD628	High CMV	1.6 mA	600 kHz ¹⁵	75 ¹⁵	1.5 mV	4	300 typ ¹⁵
AD629	High CMV, G = 1	0.9 mA	500 kHz	77 ¹²	1 mV	6	550 typ ¹²
AD626	High CMV	1.5 mA	100 kHz	55 ¹⁶	500 μV	1	250 typ
AMP03	High BW, G = 1	3.5 mA	3 MHz	85 ¹²	400 μV	NS	750 typ ¹²

monolithic dif-amp, an example

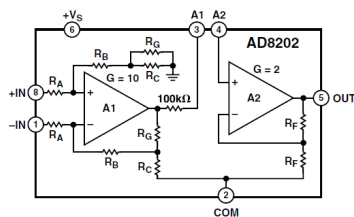


monolithic dif-amp, an example

bridge (subtractor) circuit

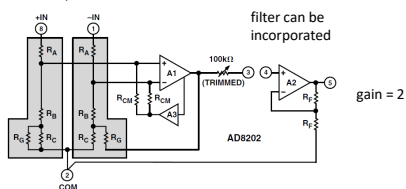


preamp gain = 10


Amplifier A3 detects the common-mode signal applied to A1 and adjusts the voltage on the matched RCM resistors to reduce the common-mode voltage range at the A1 inputs.



Master programmes in English
at Wrocław University of Technology



current shunt monitor


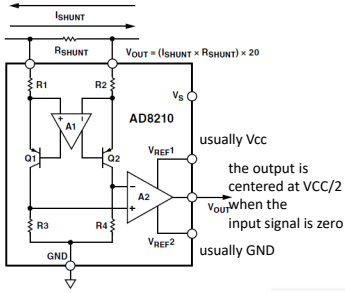





$V_{OUT} = (I_{SHUNT} \times R_{SHUNT}) \times 20$


usually V_{CC}

the output is centered at $V_{CC}/2$ when the input signal is zero

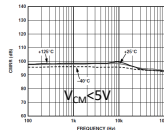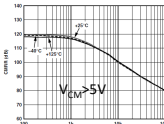
usually GND











Master programmes in English
at Wrocław University of Technology

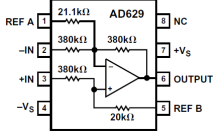


AD629




- unity-gain difference amplifier
- common-mode input voltages of up to 270 V.
- excellent CMR in the presence of high common-mode input voltages
- operate from a wide power supply range of 2.5 V to 18 V.





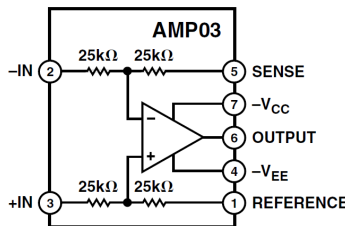
Master programmes in English
at Wrocław University of Technology








monolithic, unity-gain, 3 MHz dif-amp

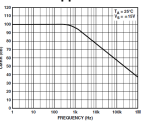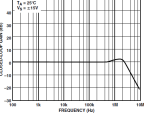basic analog building block for differential amplifier and instrumentation applications











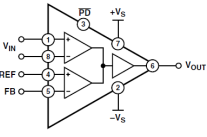

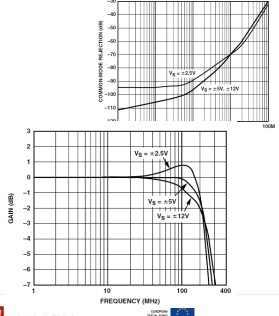Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




High Frequency Diff- Receiver/Amplifiers



- 3 dB bandwidth of 270MHz,
- 80dB CMR at 2MHz, and a 70 dB CMR at 10 MHz
- active feedback !!! – feedback do not affect the inputs













Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology


Making use of an in-amps

Application assumption:




- Dual-Supply Operation or Single-Supply Operation
- Need for True R-R Devices
- CMRR
- offset
- offset drift
- noise
- gain







Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology



Application tips

- power supply bypassing, decoupling, and stability issues
- input ground return
- center polarization of input and output (especially case of single supply)
- properly driving an in-amp's reference input
- input protection from esd and dc overload







Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Application tips

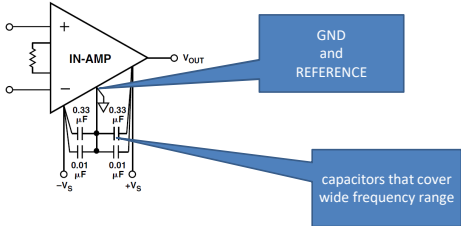
power supply bypassing, decoupling, and stability issues









Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Application tips

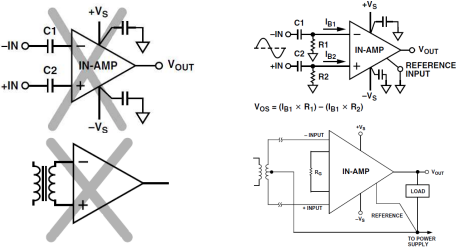
input ground return









Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology



Application tips

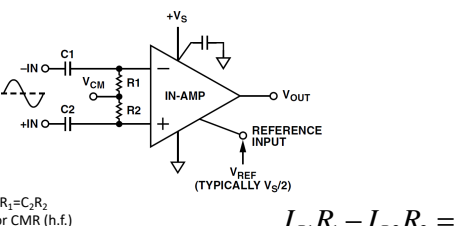center polarization of input and output









monolithic, unity-gain, 3 MHz dif-amp


basic analog building block for differential amplifier and instrumentation applications

Analogue Device
advertisement materials

 HUMAN CAPITAL
GROWTH AND WELLBEING



Wrocław University of Technology



Copyright 2014 by Wrocław University of Technology

Application tips

properly driving an in-amp's reference input

PROBLEM: R2%'S RESISTANCE CAUSES CMR ERROR AND R_{REF1} AND R_{REF2}'S ANTERIOR WINDING AN ADDITIONAL VOLTAGE REFERENCE ERROR IS INTRODUCED BY THE SHIFTING OF R2 BY R_{REF1} AND R_{REF2}.

EXTERNAL
REFERENCE
VOLTAGE

OP AMP
BUFFER

R1 EXTERNAL
REFERENCE
VOLTAGE

R2 EXTERNAL
VOLTAGE
DIVIDER

HUMAN CAPITAL
GROWTH OPPORTUNITIES

Wrocław University of Technology

EUROPEAN UNION

Wrocław University of Technology

Master programmes in English
at Wrocław University of Technology

Application tips

input protection from ESD and dc overload

6mA MAX INPUT CURRENT

internal protection

additional external protection
with Schottky diodes


additional external protection
with Schottky diodes

HUMAN CAPITAL
LAWOIS 407-000000000


Wrocław University of Technology

Wrocław University of Technology

Wrocław University of Technology




Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Application tips

gain drift

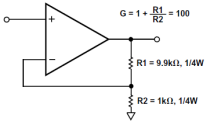


$G = 1 + \frac{R_1}{R_2} = 100$
 $R_1 = 9.9k\Omega, 1/4W$
 $R_2 = 1k\Omega, 1/4W$


Different power dissipation in R1 and R2 can cause gain drift even then temperature coefficients of both resistors are equal



Project co-financed from the EU European Social Fund




Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Application tips

gain and ofset drift

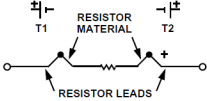


Error (voltage offset) is due to temperature difference of resistor (or any other component) terminals.


TYPICAL RESISTOR THERMOCOUPLE EMFs
 • CARBON COMPOSITION 400µV/°C
 • METAL FILM 20µV/°C
 • EVENOHM OR MANGANIN 2µV/°C
 • WIRE-WOUND 0.05µV/°C
 • RCD COMPONENTS HP-SERIES



Project co-financed from the EU European Social Fund



Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Application tips

RTI vs. RTO errors


Total Error, RTI = Input Error + (Output Error/Gain)
Total Error, RTO = (Gain * Input Error) + Output Error


VOLTAGE OFFSET	(Total RTI Error = $V_{OSI} + V_{OSO}/G$)		
Input Offset, V_{OSI}	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$	30	125
Over Temperature	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$		185
Average TC	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$	0.3	1.0
Output Offset, V_{OSO}	$V_S = \pm 15\text{ V}$	400	1000
	$V_S = \pm 5\text{ V}$		1500
Over Temperature	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$		2000
Average TC	$V_S = \pm 5\text{ V to } \pm 15\text{ V}$	5.0	15
Offset Referred to the			


Total Offset Error RTI = $V_{OSI} + (V_{OSO}/G) = 30\mu V + (400\mu V/10) = 30\mu V + 40\mu V = 70\mu V$
Total Offset Error RTO = $(G \cdot V_{OSI}) + V_{OSO} = (10 \cdot 30\mu V) + 400\mu V = 700\mu V$



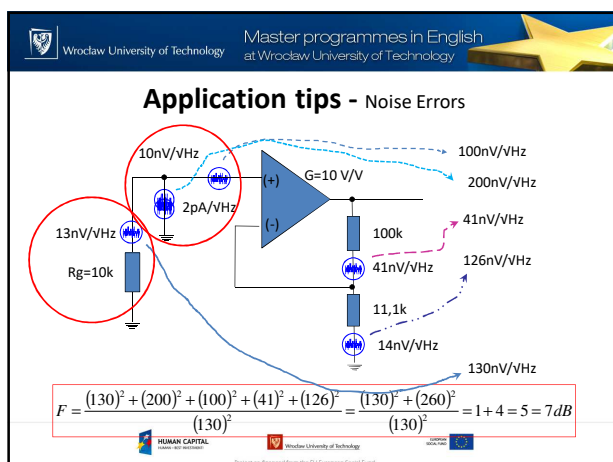Project co-financed from the EU European Social Fund



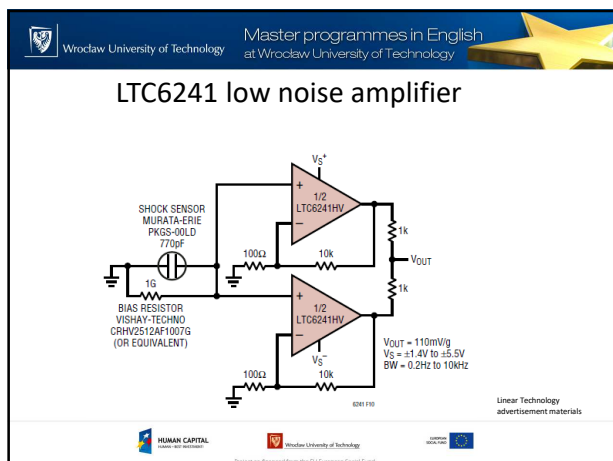

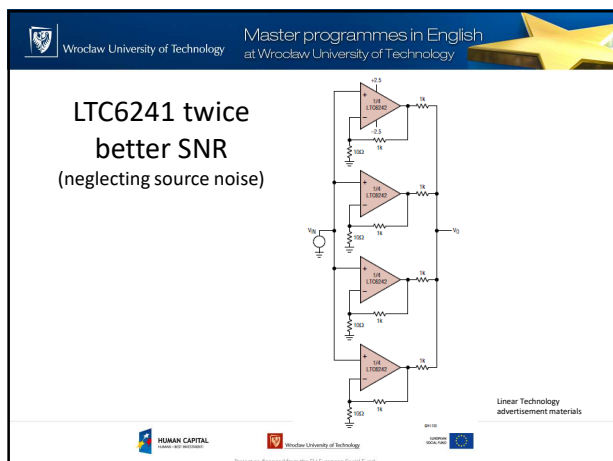

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

Application tips

Practical RFI Filters

$$B_{DF} = \frac{1}{2\pi R(2C_2 + C_1)}$$

$$B_{CM} = \frac{1}{2\pi R_1 C_1}$$

Figure 8-20 Capacitor C2 shunts C1aC1b and very effectively reduces ac CMR errors due to component mismatching.

HUMAN CAPITAL
Investing in the future

Wrocław University of Technology

Project co-financed from the EU European Social Fund

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

Application tips

Practical RFI Filters

Selecting RFI Input Filter Component Values Using a Cookbook Approach
The general rules of designing of RC input filter.

- the two series resistors
 - typical values between 2 kΩ and 10 k Ω; check if input circuit can drive these impedance,
 - these resistors should not contribute more noise than that of the in-amp itself.
- value for capacitor C2
 - C2 sets the filter's differential (signal) bandwidth; best to set this as low as possible without attenuating the input signal;a differential bandwidth of 10 times the highest signal frequency is usually adequate.
- select values for capacitors C1a and C1b; which set the common-mode bandwidth;
 - for decent ac CMR, these should be 10% the value of C2 or less,
 - The common-mode bandwidth should always be less than 10% of the in-amp's bandwidth at unity gain.

HUMAN CAPITAL
Investing in the future

Wrocław University of Technology

Project co-financed from the EU European Social Fund

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology


EMI protection result

DC offset without EMI protection is due to RECTIFICATION !!! of input RF signals.


HUMAN CAPITAL
Investing in the future

Wrocław University of Technology


Project co-financed from the EU European Social Fund



Master programmes in English
at Wrocław University of Technology




on chip emi filter

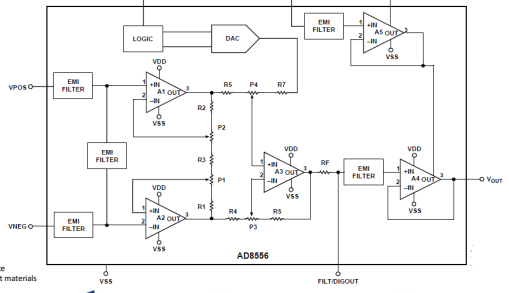


AD8556


Analog Device advertisement materials




Project co-financed from the EU European Social Fund



Master programmes in English
at Wrocław University of Technology




EMI filter with X2Y capacitor.

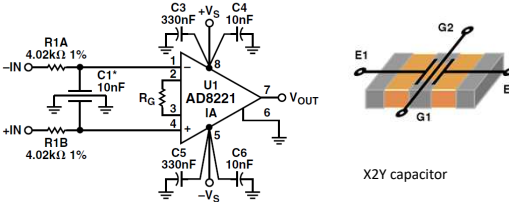


X2Y capacitor


Analog Device advertisement materials



Project co-financed from the EU European Social Fund




Master programmes in English
at Wrocław University of Technology



By the way....


X and Y capacitors in EMI filter

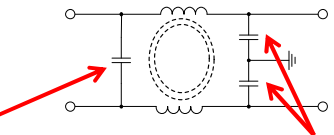


X capacitor failure could not lead to electric shock (hot to neutral)

2 Y capacitors failure could lead to electric shock if the ground connection were lost


Analog Device advertisement materials




Project co-financed from the EU European Social Fund







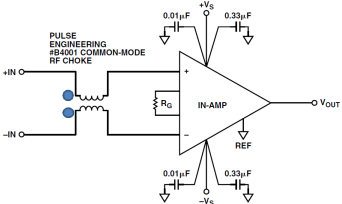Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




Common mode chock as emi filter









Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




USING LOW-PASS FILTERING TO IMPROVE SIGNAL-TO-NOISE RATIO

To extract data from a noisy measurement, low-pass filtering can be used to greatly improve the signal-to-noise ratio of the measurement by removing all signals that are not within the signal bandwidth. In some cases, band-pass filtering (reducing response both below and above the signal frequency) can be employed for an even greater improvement in measurement resolution










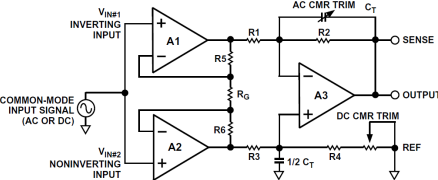
Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




External CMRR trimming




TIP: discrete design of an In-amp has usually better performance (bandwidth and CMRR)











Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




IN-AMP AND DIFF AMP APPLICATIONS CIRCUITS








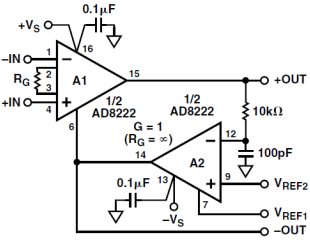Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology







A True Differential Output In-Amp Circuit




$$V_{OCM} = \frac{V_{ref1} + V_{ref2}}{2}$$

TIP: this is very useful with AD converter – V_{ref2} can be connected with U_{ref} of ADC and V_{ref1} with ADC ground so 0V of input is 1/2 value of ADC








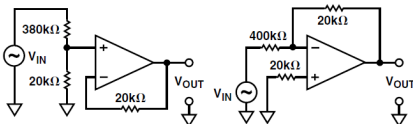Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology







High voltage measurements




TIP:

1. (on the left) single supply can be used and V_{out} is positive
2. (on the right) dual supply have to be applied, V_{out} is negative
3. If V_{in} are negative tips 1 and 2 have to be exchanged
4. power is dissipated in one resistor – self heating occurs
5. high temp gradient can cause nonlinearities , offset, drift, lower CMRR










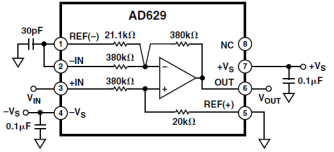
Master programmes in English
at Wrocław University of Technology




High voltage measurements improovemet




TIP: one chip – one temperature !










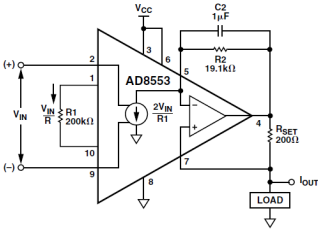

Master programmes in English
at Wrocław University of Technology




Precision Current Source










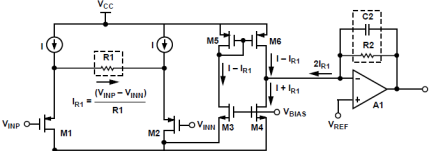Master programmes in English
at Wrocław University of Technology






$$V_{out} - V_{ref} = \frac{2R_2}{R_1} (V_+ - V_-)$$








Master programmes in English
at Wrocław University of Technology




Extremely high CMRR

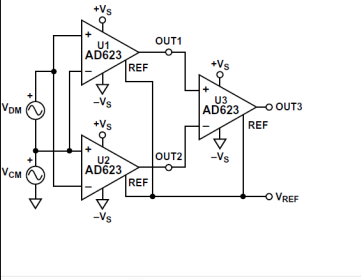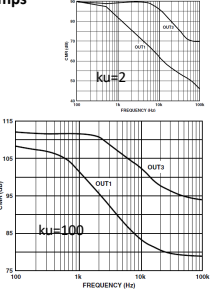
In-amp build of 3 In-amps










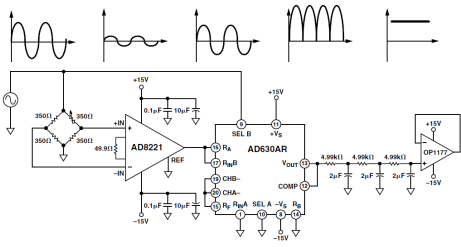

Master programmes in English
at Wrocław University of Technology




Strain gage excitation using sin signal












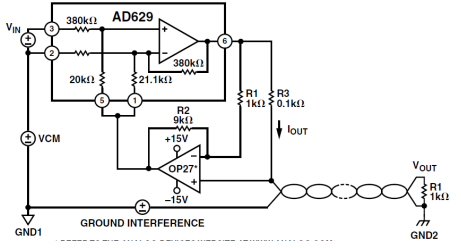

Master programmes in English
at Wrocław University of Technology




Current transmitter












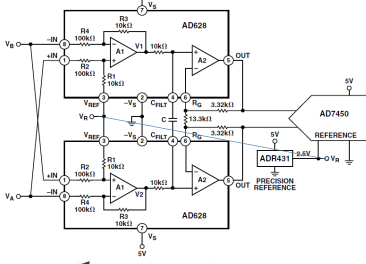
Master programmes in English
at Wrocław University of Technology




High level (+-10V) to single supply (5V) ADC




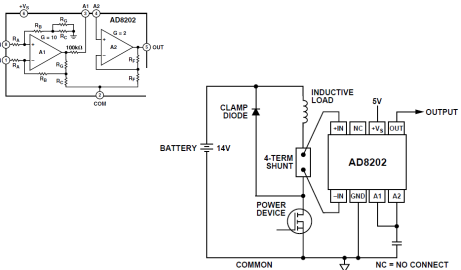
Project co-financed from the EU European Social Fund






Master programmes in English
at Wrocław University of Technology




Current probe




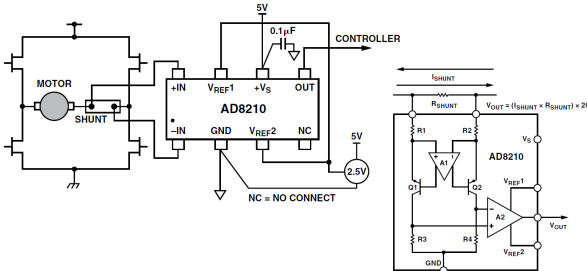
Project co-financed from the EU European Social Fund






Master programmes in English
at Wrocław University of Technology



two directional current sensor



Project co-financed from the EU European Social Fund

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

low impedance bridge excitation

* REFER TO THE ANALOG DEVICES WEBSITE AT WWW.ANALOG.COM FOR THE LATEST OP AMP PRODUCT NUMBERS AND SPECIFICATIONS.

HUMAN CAPITAL
Investing in the future

Wrocław University of Technology

Project co-financed from the EU European Social Fund

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

ECG signals acquisition

HUMAN CAPITAL
Investing in the future

Wrocław University of Technology

Project co-financed from the EU European Social Fund


Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology

Driven Shield Inputs - example


HUMAN CAPITAL
Investing in the future

Wrocław University of Technology


Project co-financed from the EU European Social Fund







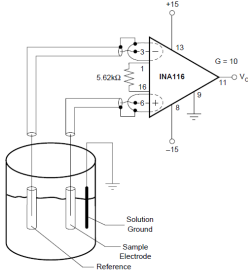Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




pH transducer












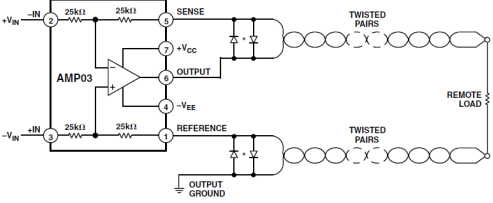

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




remote load driver












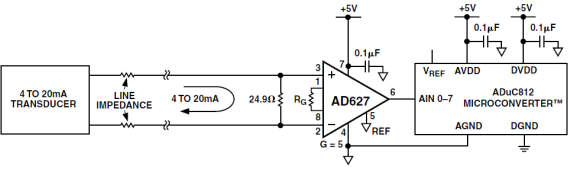

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




4-20mA loop receiver












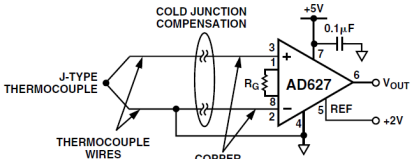

Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




termocouple transducer









Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology




summary

- Properties of an in-amp
- in-amp vs. op-amp
- in-amp vs. dif-amp
- in-amp of 3 vs. 2 op-amp
- Application tips:
 - EMI filtering
 - input protection
 - DC biasing
 - thermal noise
 - single supply problems
 - CMR trimming



Wrocław University of Technology
Master programmes in English
at Wrocław University of Technology



Test questions (an example):

- Draw two basic diagrams of a instrumentation amplifiers ?
- Compare in-amp vs. op-amp
- What wrong with the circuit (in-amp with two capacitor at the input) ? (fig.a)

